

$$I_1 = 3A \quad I_2 = \frac{7}{3}A \quad I_3 = \frac{4}{3} \quad V_0 = 6V$$

K.V.L For loop (4)

$$\sum V_{\text{rise}} = \sum V_{\text{drop}}$$

$$V_x = 6V$$

$$0 = -4(I_0) + 12 - 6(I_2) + V_x$$

Power balance ()

$$P \Rightarrow \text{watt} \Rightarrow P = VI$$

* For resistance $V = IR$

$$R \Rightarrow P = VI = I^2R = \frac{V^2}{R}$$

$$\text{Voltage source } (+) \Rightarrow P = VI$$





$$\text{Current source } (\rightarrow) \Rightarrow P = VI$$

$$R \Rightarrow \text{Consume Power}$$

$$I \rightarrow (+) \Rightarrow \text{Consume Power}$$

$$(+)\leftarrow I \Rightarrow \text{Supply Power}$$

* For the Example

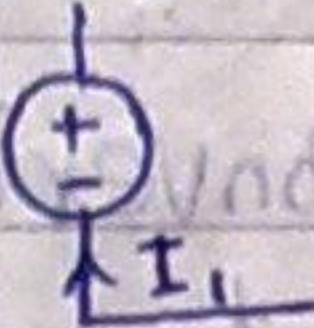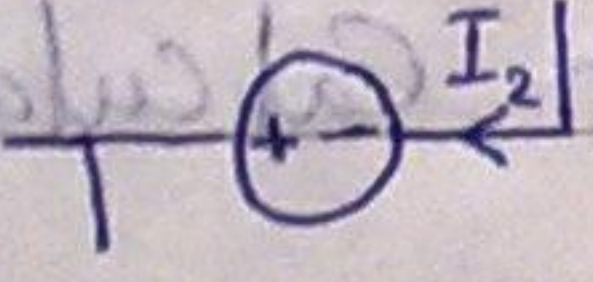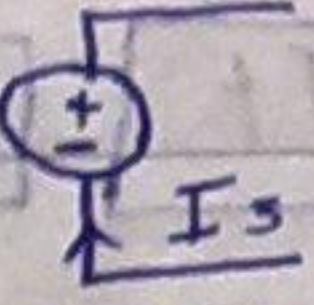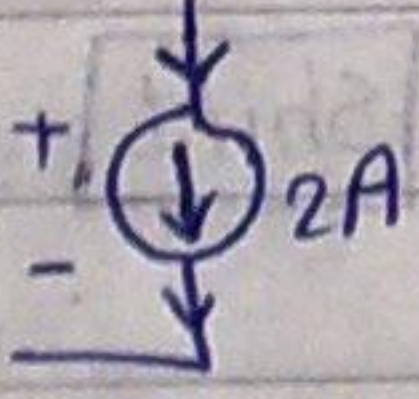element	Power (watt)	Consume or Supply
$2\ \Omega$	$2 \times (3)^2 = 18$	Consume
$3\ \Omega$	$3 \times \left(\frac{4}{3}\right)^2 = \frac{16}{3}$	Consume
$4\ \Omega$	$4 \times (1)^2 = 4$	Consume
$6\ \Omega$	$6 \times \left(\frac{7}{3}\right)^2 = \frac{98}{3}$	Consume
12V 	$12 \times 3 = 36$	Supply
12V 	$12 \times \frac{7}{3} = 28$	Supply
$V_s = 6\text{V}$ 	$6 \times \frac{4}{3} = 8$	Supply
$V_x = 6\text{V}$ 	$6 \times 2 = 12$	Consume

Complex numbers


$$A = a_1 + j a_2 \rightarrow \text{Rect. Form}$$

$$A = |A| \angle \theta \rightarrow \text{Polar Form}$$

i.e

$$A = 3 + j 4 \text{ Rect. Form}$$
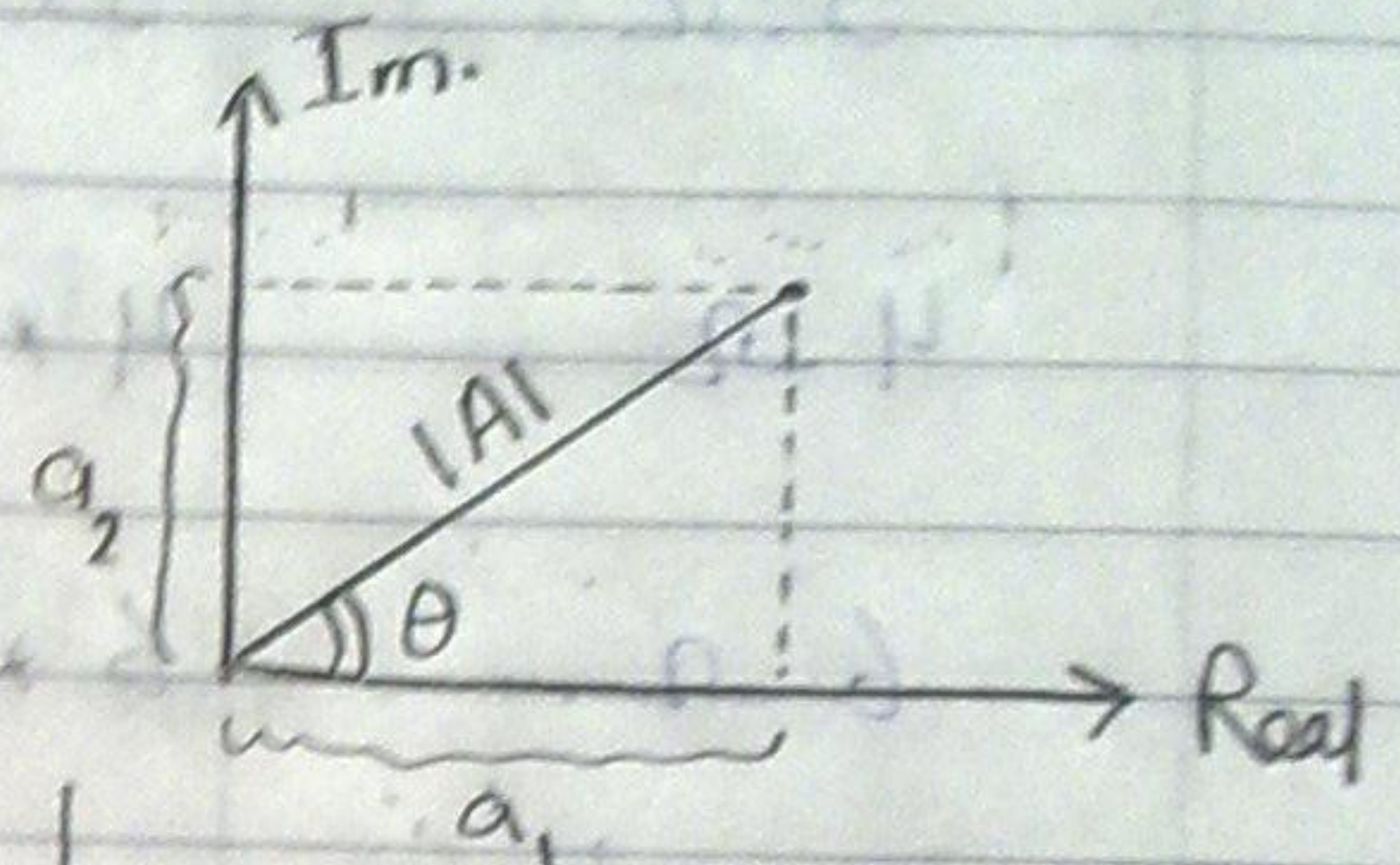
$$A = 5 \angle 53.13 \text{ Polar Form}$$



Rec	Polar
3	3 ∠ 0
-3	3 ∠ ±180
j 3	3 ∠ 90
-j 3	3 ∠ -90
-3 - j 3	3√2 ∠ 45

To convert From Rect. to Polar on Calculator

Shift + \angle real no. a_1

⇒ Shift) \angle Im. no. a_2

* $B + A$
* $B - A$ } addition or sub. as Rect. Form

$$* B * A = |A| \angle \theta_1 \quad |B| \angle \theta_2 = |AB| \angle \theta_1 + \theta_2$$

$$* \frac{B}{A} = \frac{|B| \angle \theta_2}{|A| \angle \theta_1} = \left| \frac{B}{A} \right| \angle \theta_2 - \theta_1$$